

Concepts of Electricity

by: Dr. Prosper NDIZIHIWE, INES Ruhengeri

Concepts and laws

➤ **1.1 Introduction: Current and Voltage**

1.2 Circuit Elements

1.3 Power and Energy


1.4 Laws: Ohm's Law, Kirchhoff's Laws

1.5 Transformations

1.1 Introduction: Current and Voltage

- An **electronic circuit** is an interconnection of electrical elements.

Fig 1.1.1: Electric circuit of a radio transmitter

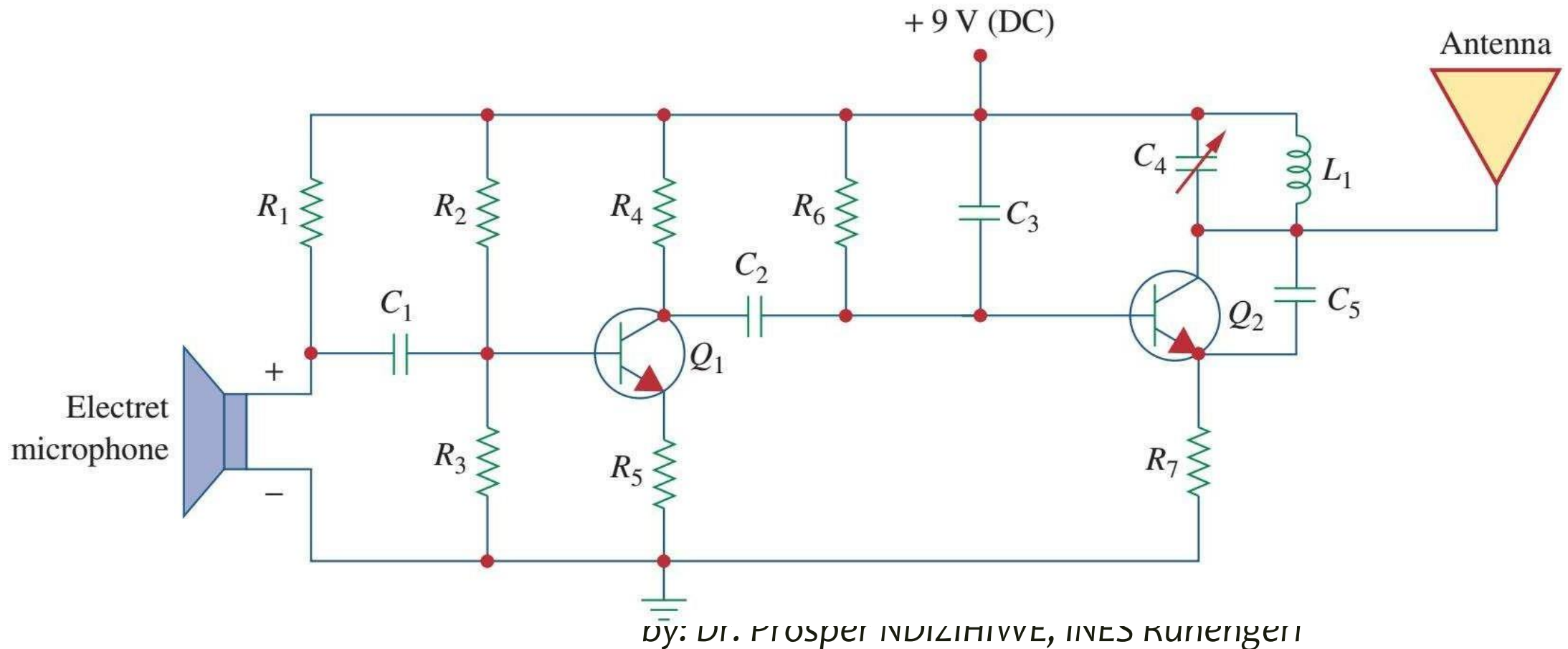

1.1 Introduction: Current and Voltage

- **Charge** is an electrical property of the atomic particles, measured in coulombs (C).
- **Electric current** is the time rate of change of charge, measured in amperes (A).

$$i = \frac{dq}{dt} \begin{cases} i : \text{current} \\ q : \text{charge} \\ t : \text{time} \end{cases}$$

- 1 ampere = 1 coulomb/second.


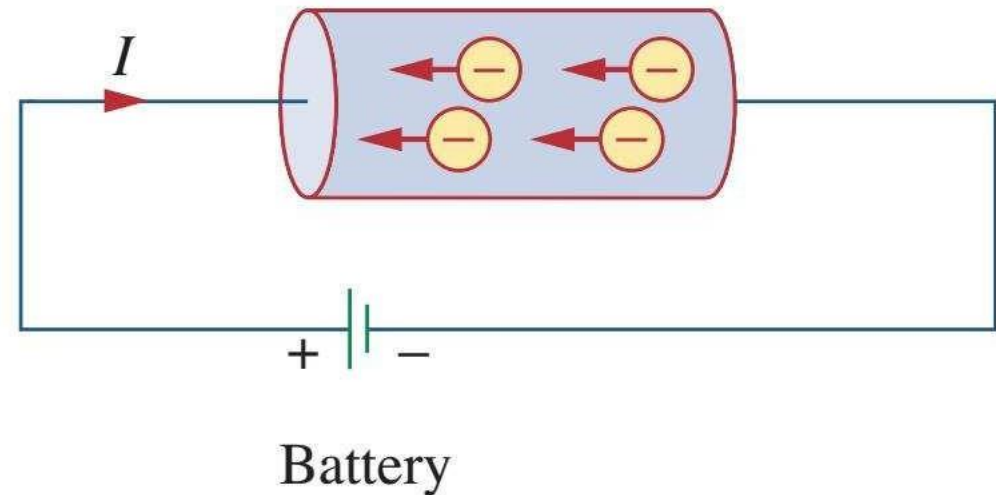



Fig 1.1.2: Electric current due to flow of electronic charge in a conductor

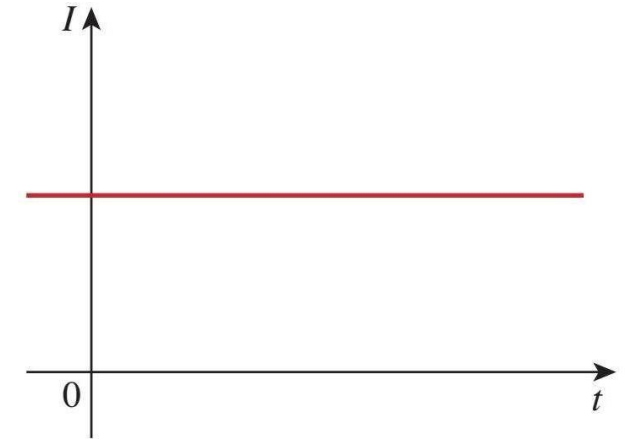1.1 Introduction: Current and Voltage

- A **direct current (dc)** is a current that remains constant with time.
- An **alternating current (ac)** is a current that varies with time.
- The direction of current flow is the direction of positive charge movement.



(a)

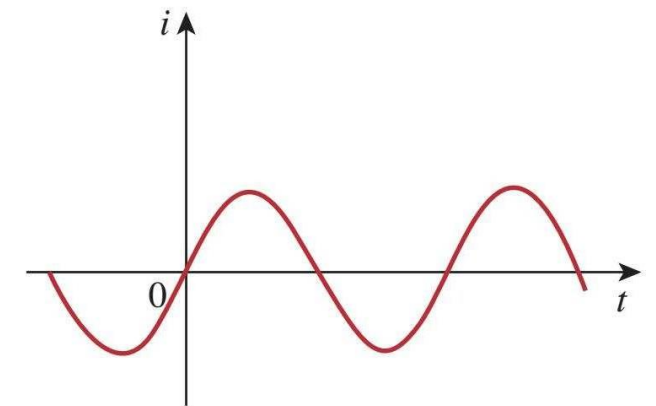

(b)

*Fig 1.1.3: Two common types of currents:
(a) direct current, (b) alternating current*

1.1 Introduction: Current and Voltage

- **Voltage** (or **potential difference**) is the energy required to move a unit charge through an element.
- Voltage is measured in volts (V).

$$u_{ab} = \frac{dw}{dq} \begin{cases} u: \text{voltage (V)} \\ w: \text{energy (joules - J)} \\ q: \text{charge (C)} \end{cases}$$

- 1 volt = 1 joule/coulomb = 1 Nm/coulomb.

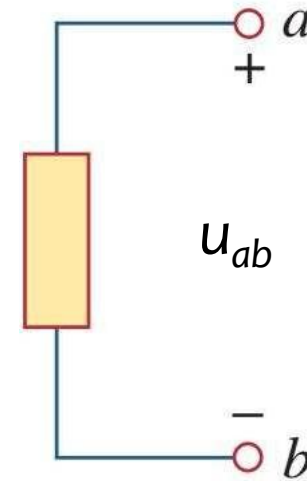


Fig 1.1.4: Polarity of voltage u_{ab} .

1.1 Introduction: Current and Voltage

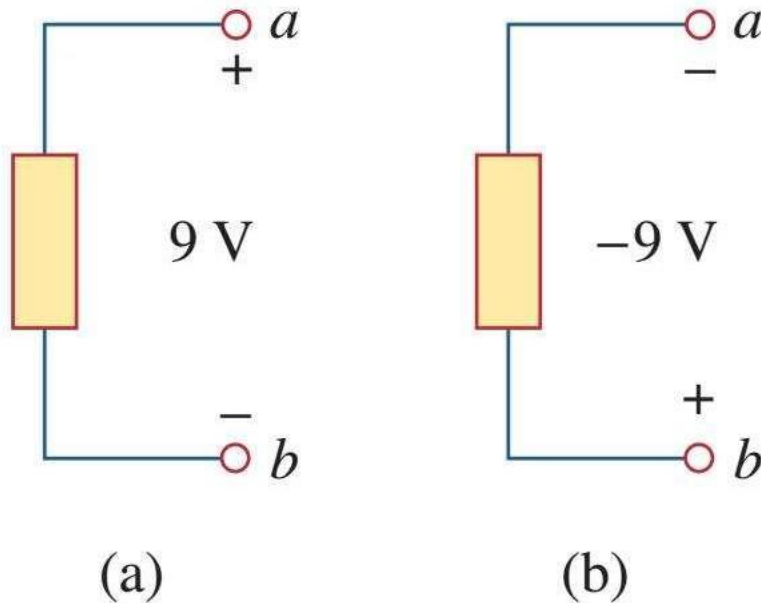


Fig 1.1.5: Two equivalent representations of the same voltage u_{ab} .

- A **dc voltage** is a constant voltage.
- An **ac voltage** is a time-varying voltage.

Concepts and laws

1.1 Introduction: Current and Voltage

➤ **1.2 Circuit Elements**

1.3 Power and Energy

1.4 Laws: Ohm's Law, Kirchhoff's Laws

1.5 Transformations

1.2 Circuit Elements

- An **ideal independent source** is an active element that provides a specified voltage or current that is completely independent of other circuit elements.
- There are two kinds of independent sources: **independent voltage source** and **independent current source**.

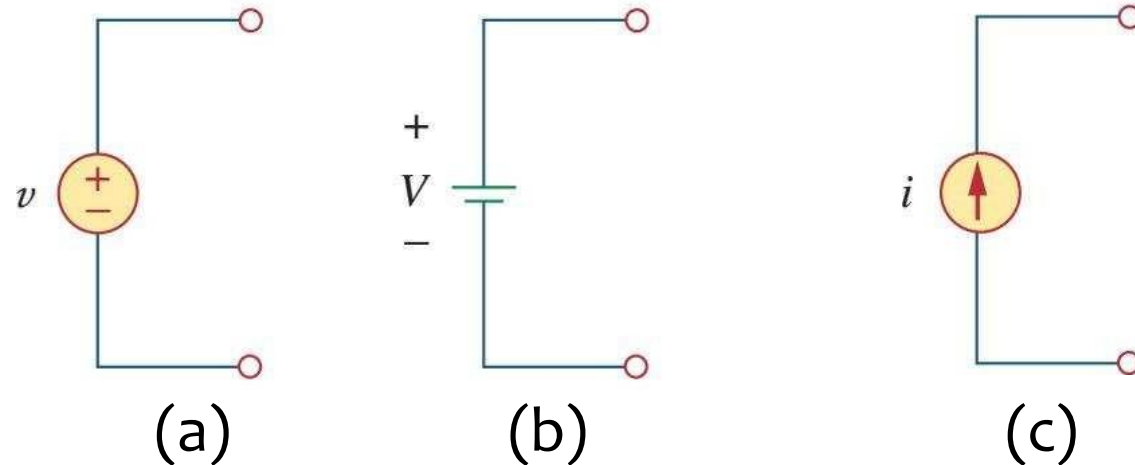


Fig 1.2.1: Symbols for independent sources: (a) used for ac and dc voltage; (b) used for dc voltage; (c) used for current source.

1.2 Circuit Elements

- An **ideal dependent** (or **controlled**) **source** is an active element in which the source quantity is controlled by another voltage or current.
- There are four possible types of dependent sources, namely:
 - i. A voltage-controlled voltage source (VCVS).
 - ii. A current-controlled voltage source (CCVS).
 - iii. A voltage-controlled current source (VCCS).
 - iv. A current-controlled current source (CCCS).

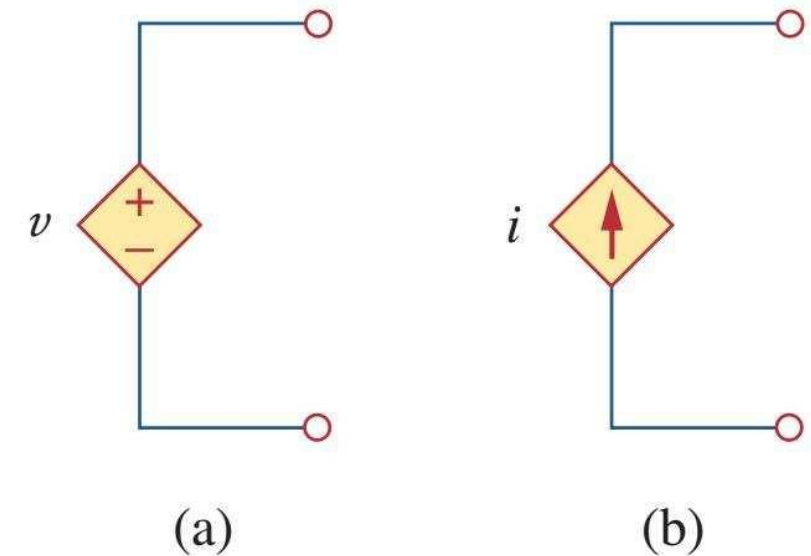


Fig 1.2.2: Symbols for: (a) dependent voltage source, (b) dependent current source.

1.2 Circuit Elements

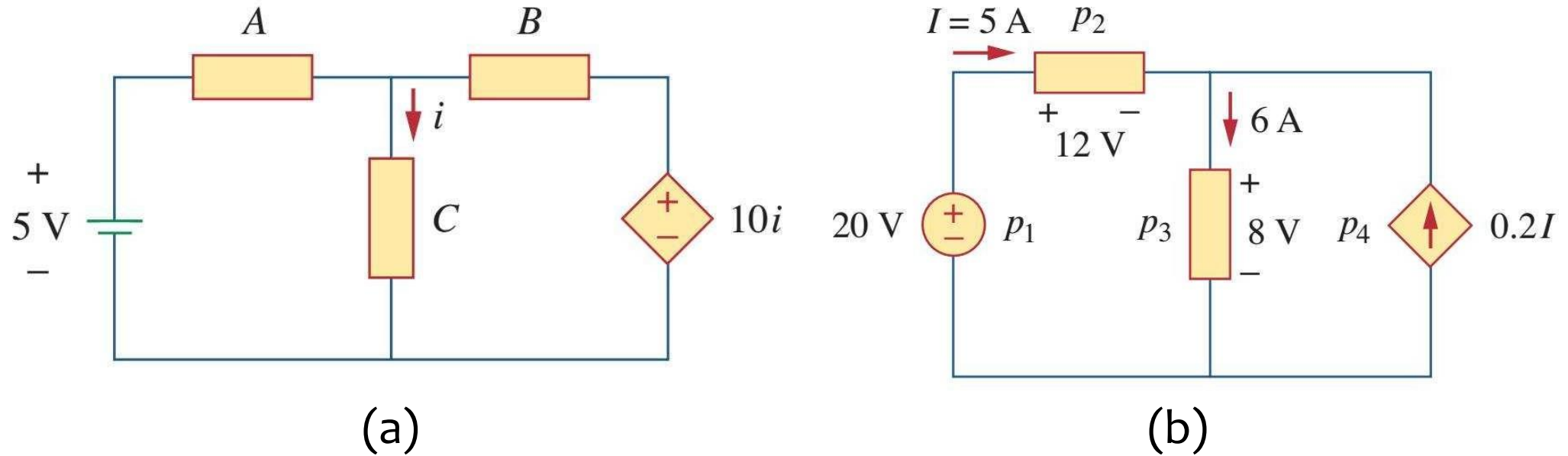


Fig 1.2.3: Examples of: (a) CCVS, (b) CCCS.

1.2 Circuit Elements

- A **resistor** is a passive electrical component with the primary function to limit the flow of electric current. Resistors are measured in Ohms (Ω).


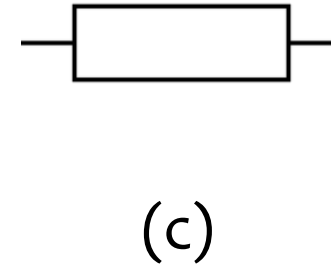
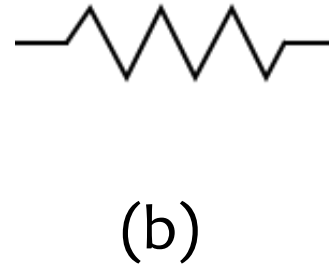
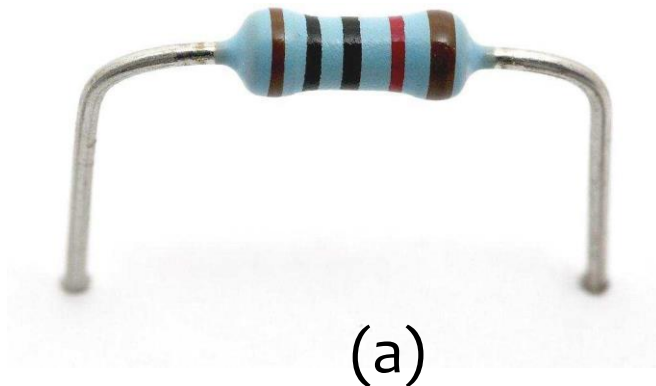
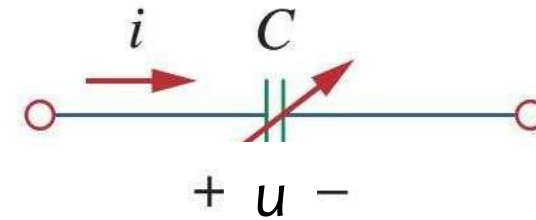
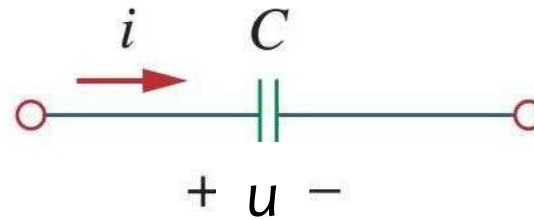


Fig 1.2.4: (a) A common kind of resistor, (b) Resistor symbol - ANSI standard, (c) another resistor symbol

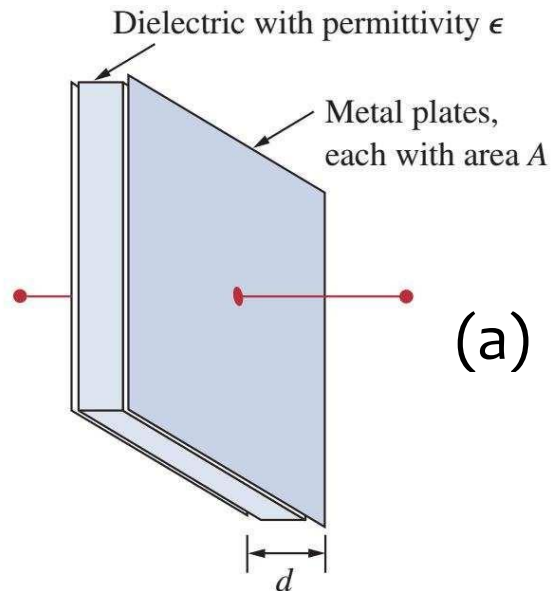1.2 Circuit Elements

- A **capacitor** consists of two conducting plates separated by an insulator (or dielectric).
- **Capacitance** is the ratio of the charge on one plate of a capacitor to the voltage difference between the two plates, measured in farads (F).




1.2.5: (a) A typical capacitor, (b) fixed capacitor symbol, (c) variable capacitor symbol

$$C = \frac{\epsilon A}{d}; \quad i_c = C \frac{du_c}{dt}$$

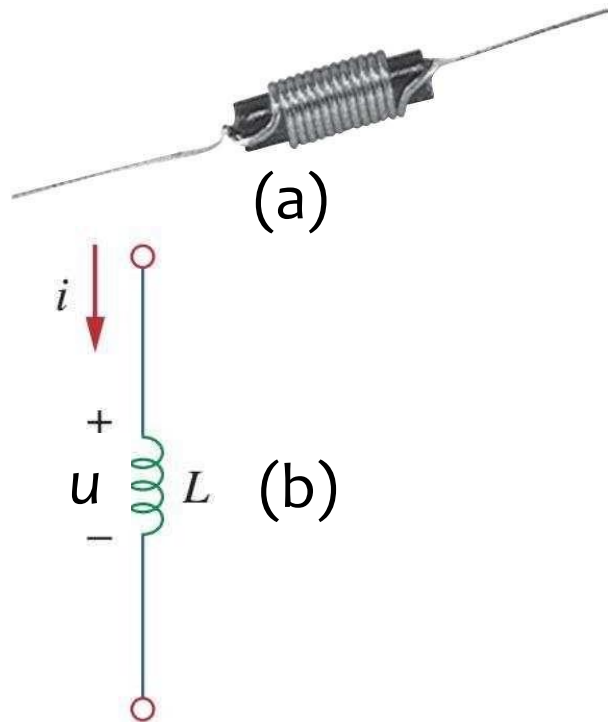1.2 Circuit Elements

- An **inductor** consists of a coil of conducting wire.
- **Inductance** is the property whereby an inductor exhibits opposition to the change of current flowing through it, measured in henrys (H).



$$L = \frac{N^2 \mu A}{l} \begin{cases} N: \text{number of turns} \\ \mu: \text{permeability of the core} \\ A: \text{cross-sectional area} \\ l: \text{length of the coil} \end{cases}$$


$$u_L = L \frac{di_L}{dt}$$

Fig 1.2.6: (a) A typical inductor,
(b) fixed inductor symbol


by: Dr. Prosper NDIZIHIWE, INES Ruhengeri

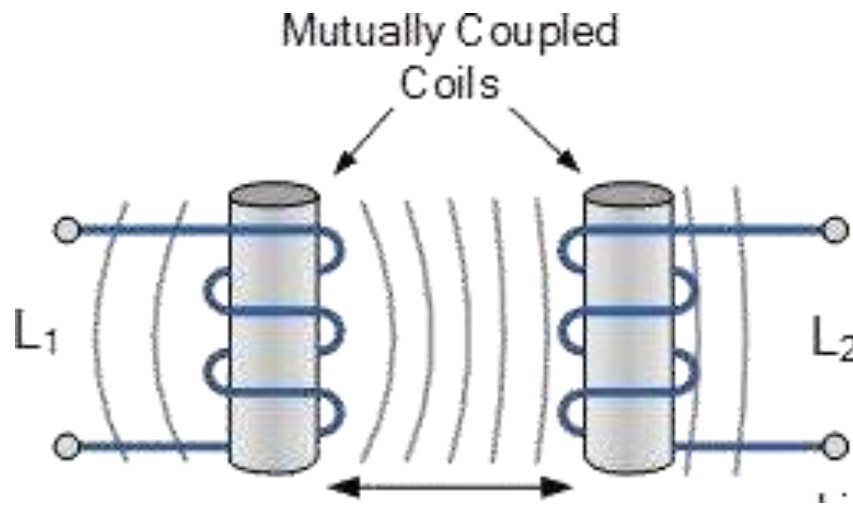1.2 Circuit Elements

- When two or more coils are magnetically linked together by a common magnetic flux they are said to have the property of **Mutual Inductance**.


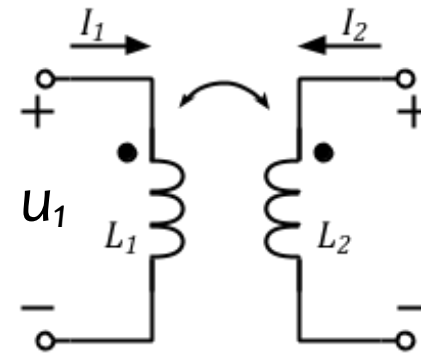
$$M = k_c \sqrt{L_1 L_2} \quad 0 \leq k_c \leq 1$$





$$\begin{cases} u_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ u_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \end{cases}$$

Fig 1.2.7: Mutual inductance and its symbol

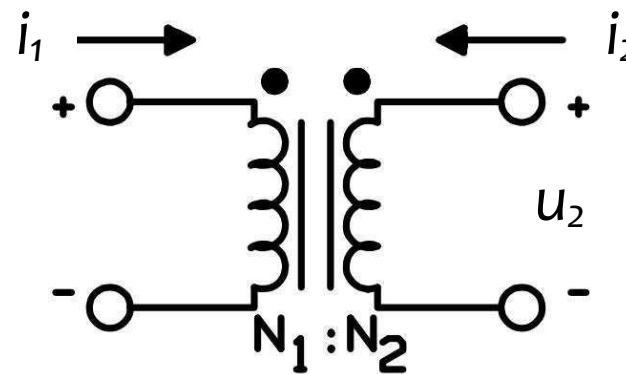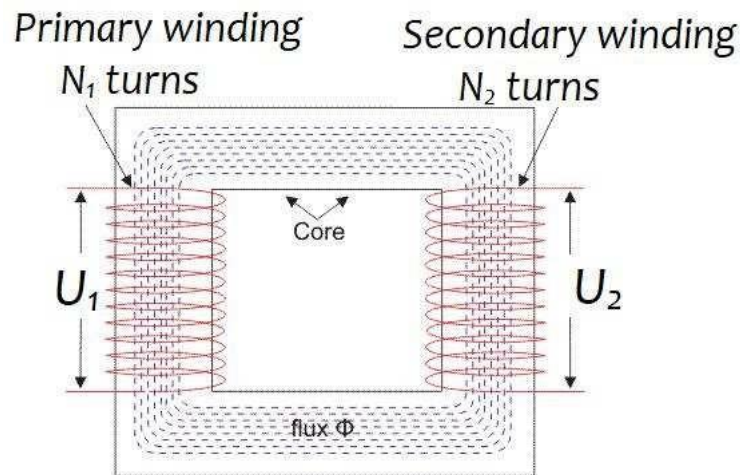1.2 Circuit Elements

- **Electrical transformer** is a static device which transforms electrical energy from one circuit to another without any direct electrical connection, with the help of mutual inductance.
- An **ideal transformer** is an imaginary transformer which does not have any loss in it.



$$\begin{cases} \frac{u_1}{u_2} = \frac{N_1}{N_2} \\ \frac{i_1}{i_2} = -\frac{N_2}{N_1} \end{cases}$$

Fig 1.2.8: (Ideal) transformer and its symbol

Concepts and laws

1.1 Introduction: Current and Voltage

1.2 Circuit Elements

➤ **1.3 Power and Energy**

1.4 Laws: Ohm's Law, Kirchhoff's Laws

1.5 Transformations

1.3 Power and Energy


- **Power** is the time rate of expending or absorbing energy, measured in watts (W).

- Instantaneous power: $p(t) = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = u(t) \cdot i(t)$

$$P = \frac{1}{T} \int_0^T p(t) dt$$

- Average power:
 - $P > 0$: absorbing power
 - $P < 0$: supplying power
- **Law of conservation of energy:**

$$\sum P = 0$$

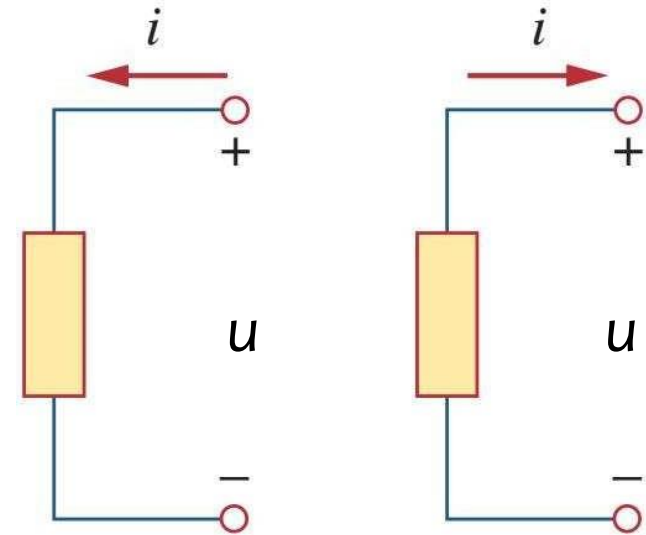

in a circuit

1.3 Power and Energy

(a)

Fig 1.3.8: (a)

$$p = u.i$$

(b)

$$(b) \ p = -u.i$$

1.3 Power and Energy

- **Energy** is the capacity to do work, measured in joules (J).

$$w = \int_{t_0}^t p dt = \int_{t_0}^t u \cdot i dt$$

- 1Wh (watt-hours) = 3600J; 1KWh = 3600000J.
- Passive elements (R, L, C, transformer, etc): $W > 0$.
- Active elements (such as independent voltage or current sources): $W < 0$.


Example 1.3.1: A family in the rural area uses a 40W light bulb in 6 hours per day, the electricity price is 89/KWh. How much does the electricity cost within a month (30 days)?

1.3 Power and Energy

Elements	Average Power	Energy
Resistor	$P_R = Ri^2$	$W_R = R \int_{t_0}^t i^2 dt$
Capacitor	$P_C = 0$	$W_C = \frac{1}{2} Cu_c^2$
Inductor	$P_L = 0$	$W_L = \frac{1}{2} Li_L^2$

1.3 Power and Energy

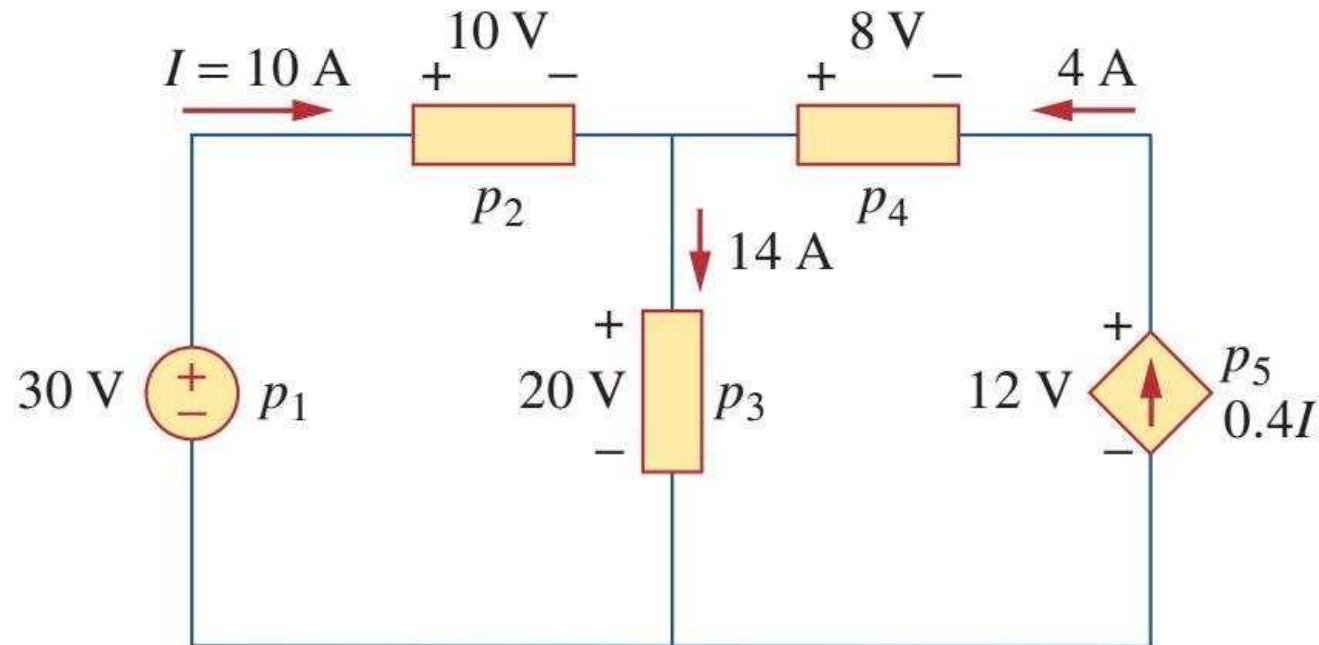- Example 1.3.2: Find the power of all elements in the circuit below:



Concepts and laws

1.1 Introduction: Current and Voltage

1.2 Circuit Elements

1.3 Power and Energy

➤ **1.4 Laws: Ohm's Law, Kirchhoff's Laws**

1.5 Transformations


1.4 Laws

- **Ohm's law** states the voltage u across a resistor is directly proportional to the current i flowing through that resistor.

$$u(t) = R \cdot i(t)$$

- A **short circuit** is a circuit element with resistance approaching zero.
- A **open circuit** is a circuit element with resistance approaching infinity.
- Power dissipated by a resistor: $p = u(t) \cdot i(t) = i^2(t)R = u^2(t)/R$.
- **Conductance** is the ability of an element to conduct electric current, it is measured in mhos ($\text{M}\Omega$) or siemens (S).

$$G = \frac{1}{R} = \frac{i}{u}$$

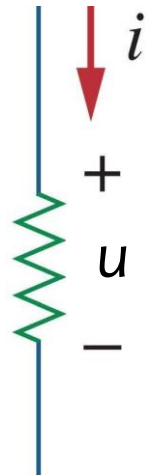

1.4 Laws

- A **branch** represents any two-terminal element.
- A **node** is the point of connection between two or more branches.
- A **loop** is a closed path in a circuit where there is no node which is traversed twice except the initial point.
- A **mesh** is a loop with no path inside.


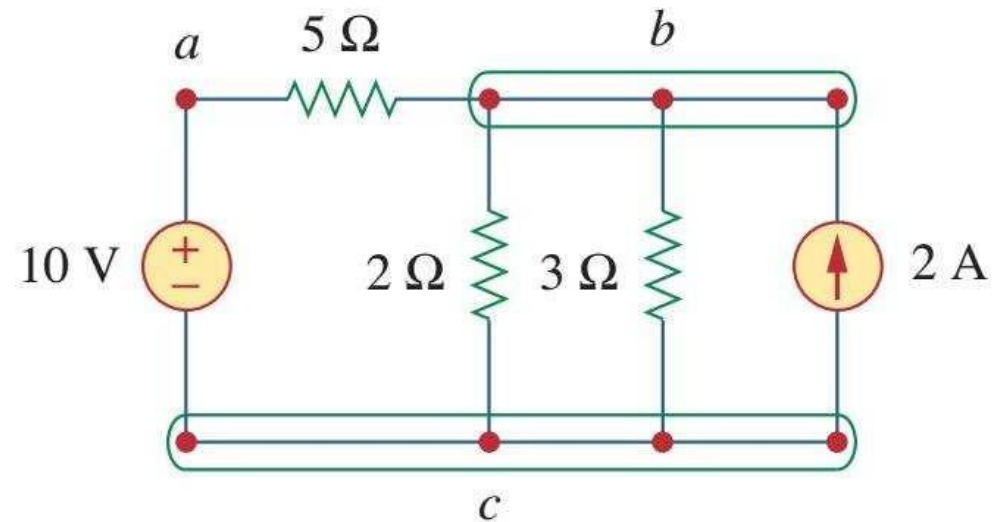


Fig 1.4.1: Branches, nodes, loops and meshes.

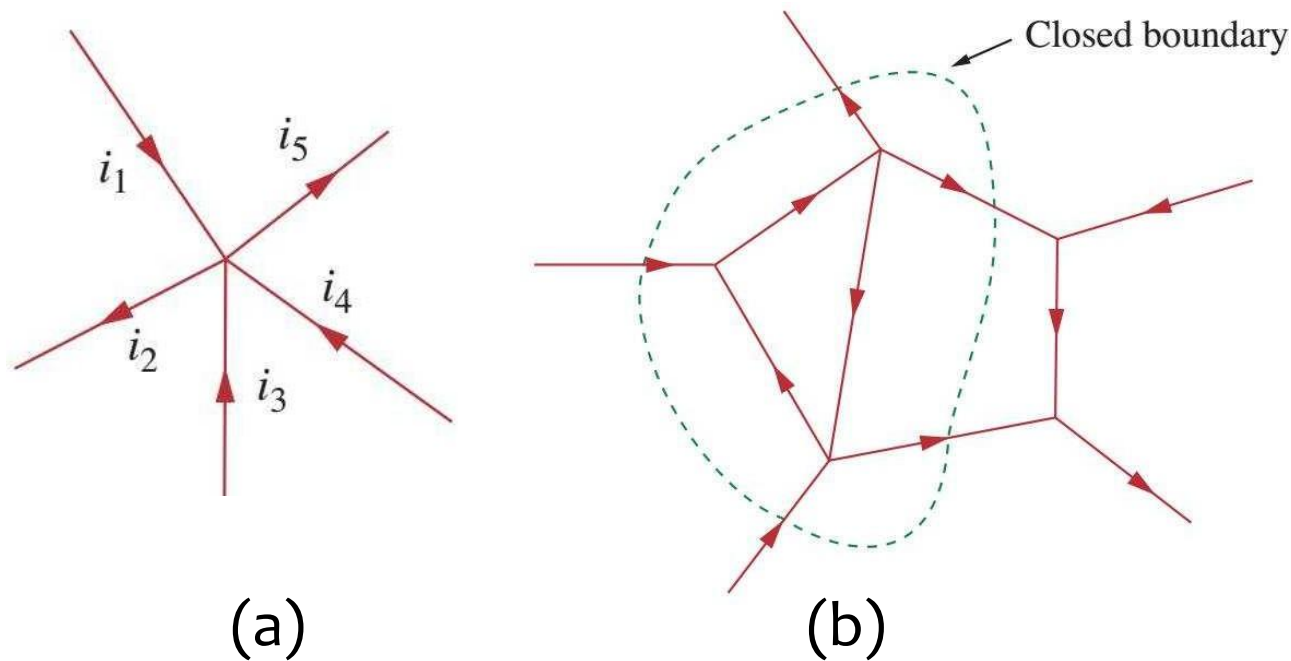1.4 Laws

- **Kirchhoff's current law (KCL)** states that the algebraic sum of currents entering a node (or a closed boundary) is zero.




For the node in Fig 1.4.2
 $i_1 + (-i_2) + i_3 + i_4 + (-i_5) = 0$
or $i_1 + i_3 + i_4 = i_2 + i_5$

Fig 1.4.2: (a) Currents at a node (b)
Applying KCL to a closed boundary

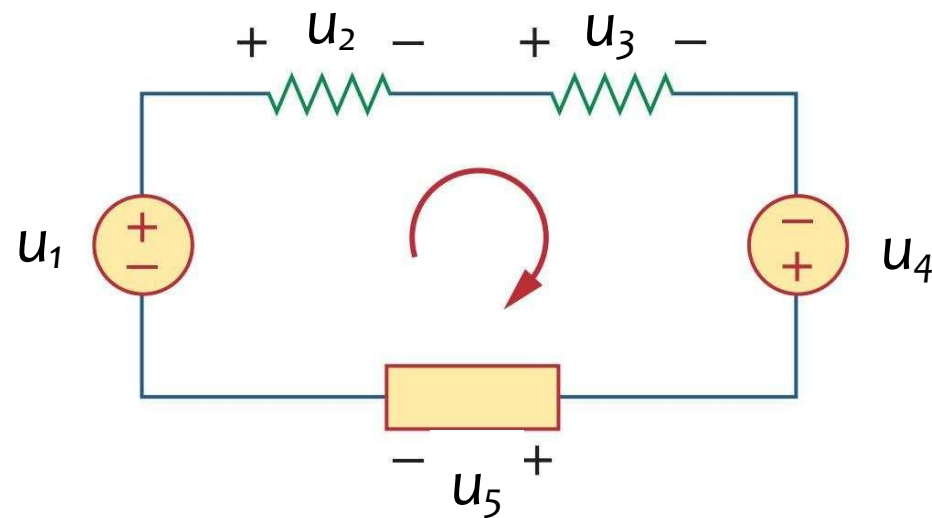
1.4 Laws

- **Kirchhoff's voltage law (KVL)** states that the algebraic sum of all voltages around a loop is zero.



$$-u_1 + u_2 + u_3 - u_4 + u_5 = 0$$
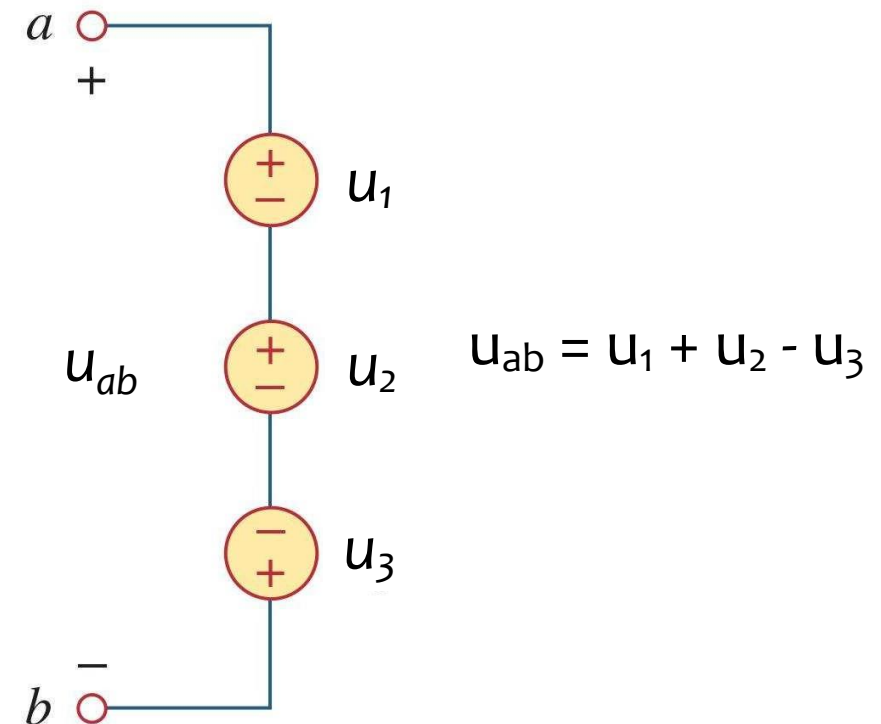
$$\Leftrightarrow u_1 + u_4 = u_2 + u_3 + u_5$$



$$u_{ab} = u_1 + u_2 - u_3$$

Fig 1.4.3: Illustrating KVL

1.4 Laws

- Example 1.4.1: Find u_1 and u_2 in the circuit of Fig 1.4.4 (a).
- Example 1.4.2: Determine u_x and u_o in the circuit of Fig 1.4.4 (b).

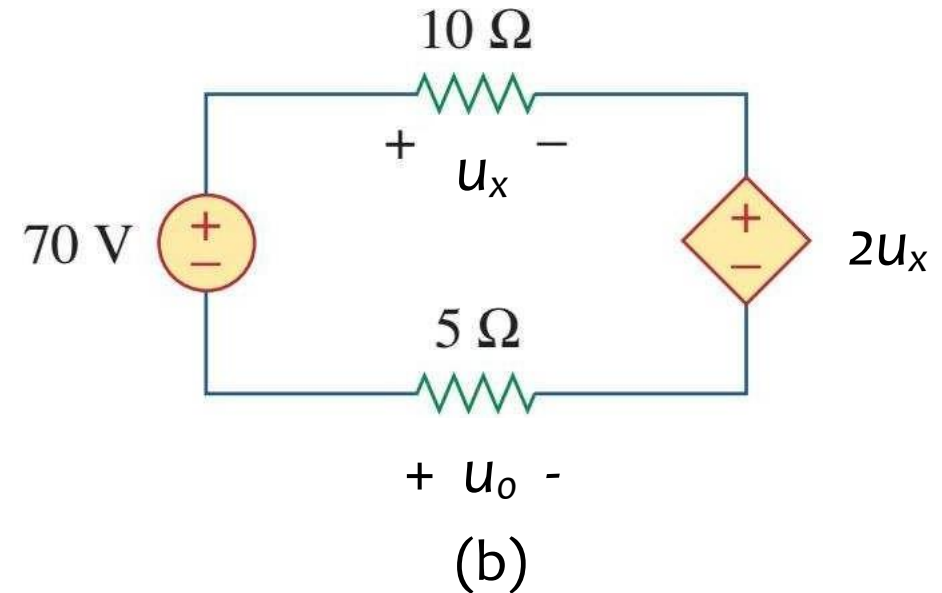
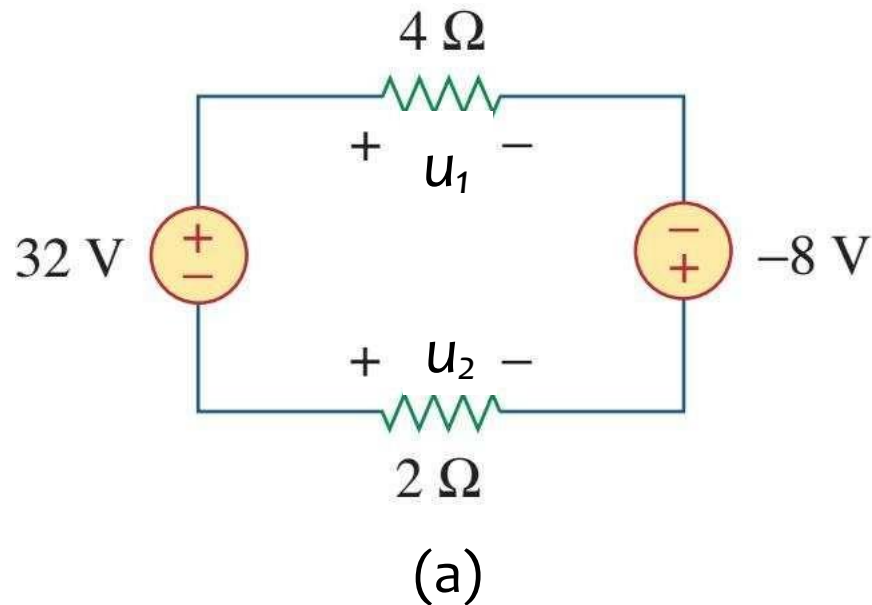


Fig 1.4.4: Circuit for Example 1.4.1 and Example 1.4.2

1.4 Laws

- Example 1.4.3: Find i_o and u_o in the circuit of Fig 1.4.5, then calculate the power of all elements.

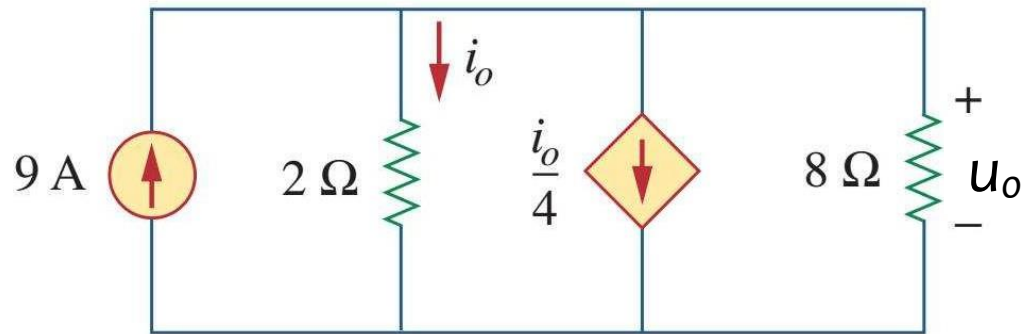


Fig 1.4.5: Circuit for Example 1.4.3

Concepts and laws

1.1 Introduction: Current and Voltage

1.2 Circuit Elements



1.3 Power and Energy

1.4 Laws: Ohm's Law, Kirchhoff's Laws

➤ **1.5 Transformations**

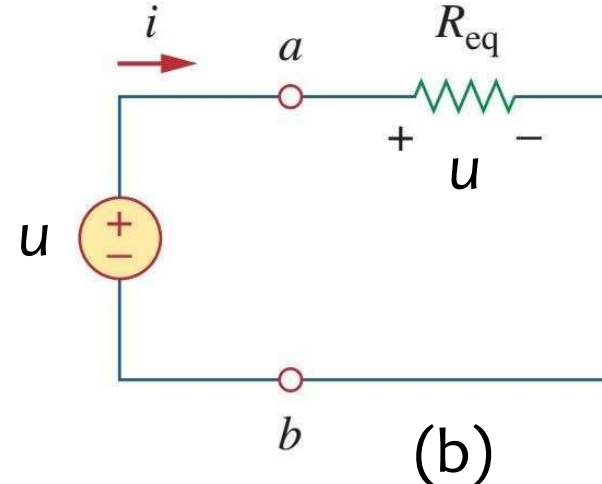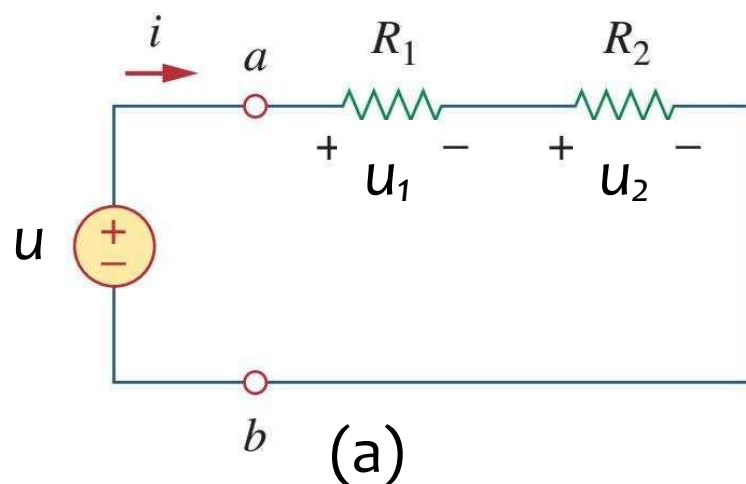1.5 Transformation

- The **equivalent resistance** of any number of resistors connected in series is the sum of the individual resistances.



$$R_{eq} = R_1 + R_2$$

Fig 1.5.1: (a) A circuit with two resistors in series and (b) equivalent circuit

- Voltage division: $u_1 = \frac{R_1}{R_1 + R_2} u$; $u_2 = \frac{R_2}{R_1 + R_2} u$;

1.5 Transformations

- The **equivalent resistance** of any number of resistors connected in series is the sum of the individual resistances.

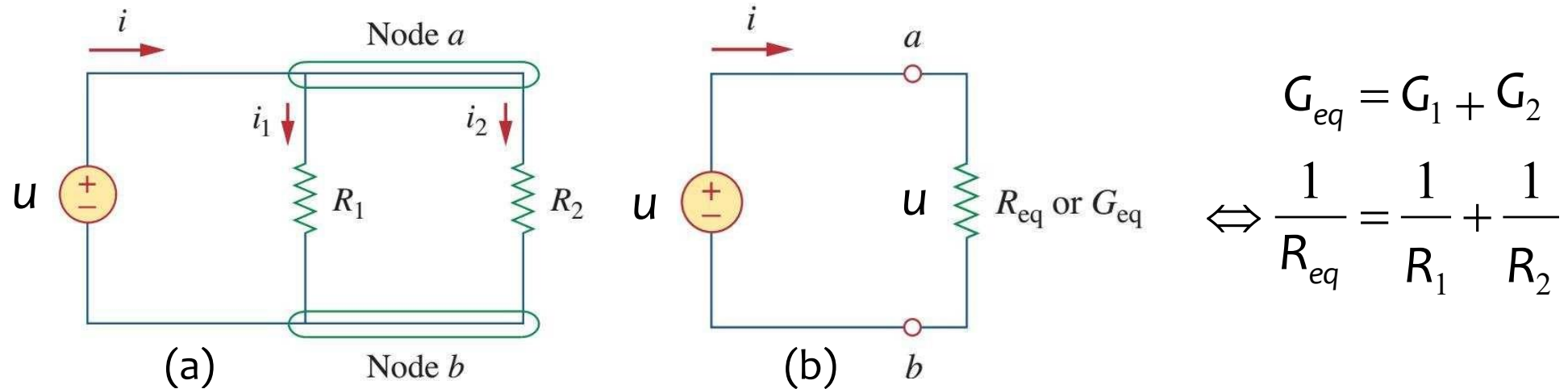


Fig 1.5.2: (a) A circuit with two resistors in parallel and (b) equivalent circuit

- Current division:
$$i_1 = \frac{R_2}{R_1 + R_2} i; \quad i_2 = \frac{R_1}{R_1 + R_2} i;$$

1.5 Transformations

■ Wye-Delta (Y-Δ) transformations:

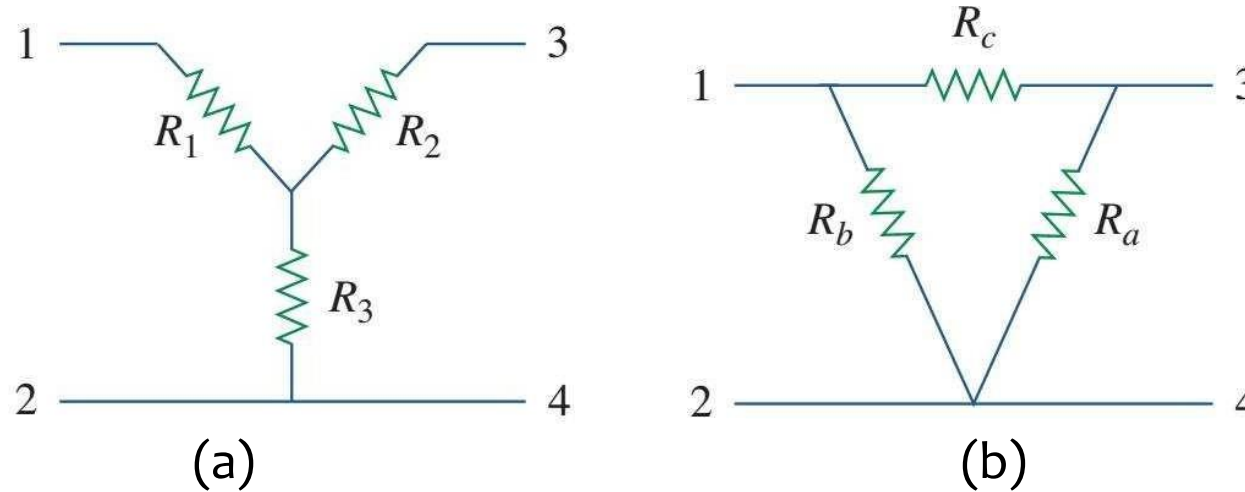


Fig 1.5.3: (a) Y network and (b) Δ network

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

1.5 Transformations

Example 1.5.1: For the bridge network in Fig 1.5.4, find R_{ab} and i .

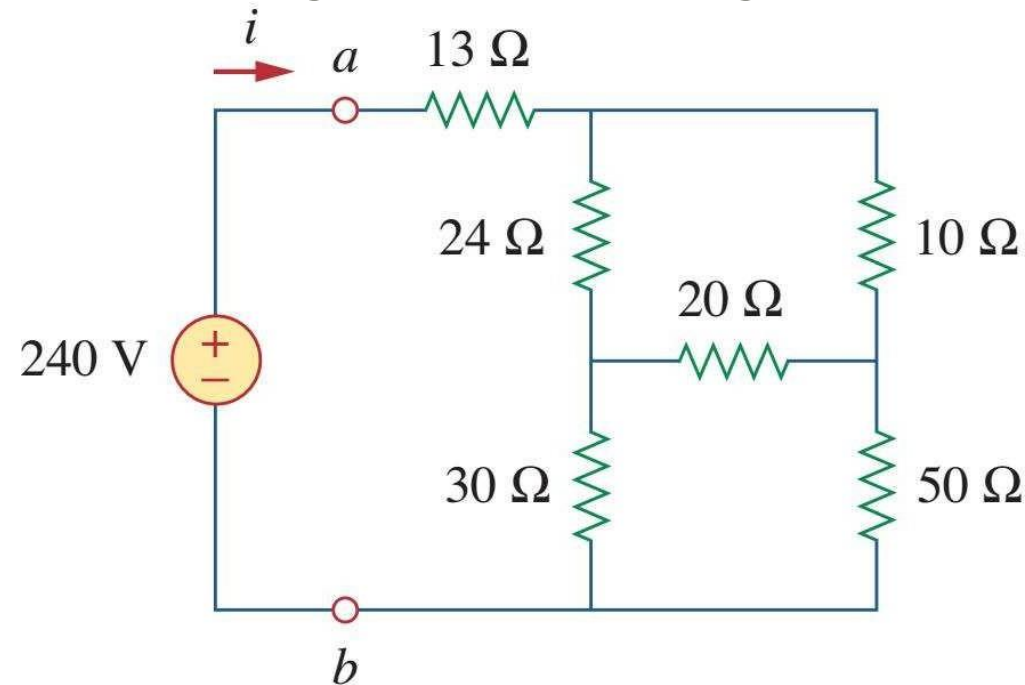





Fig 1.5.4: Circuit for Example 1.5.1

Answer: 40Ω , 6A.

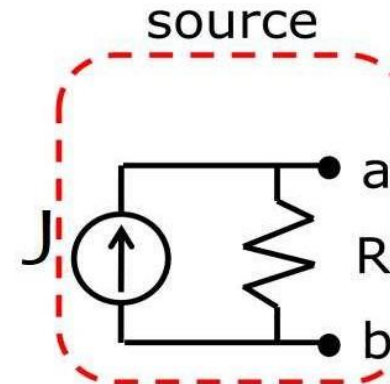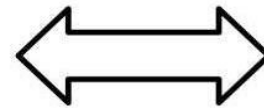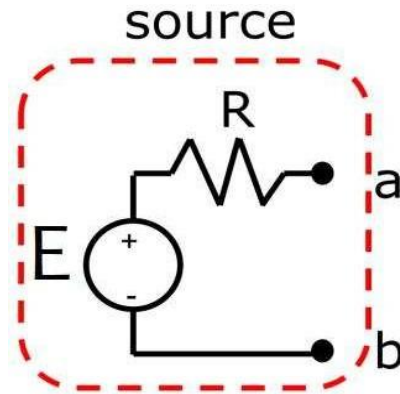1.5 Transformations

■ Source transformations:

'E' is usually used
to denote a
voltage source



'J' is usually used
to denote a
current source

Fig 1.5.5: Source transformations

- Two circuits in Fig 1.5.5 will be equivalent if and only if **$E = J.R$** .

1.5 Transformations

Example 1.5.2: In the circuit shown in Fig 1.5.6, determine u_x and the power absorbed by the 12Ω resistor.

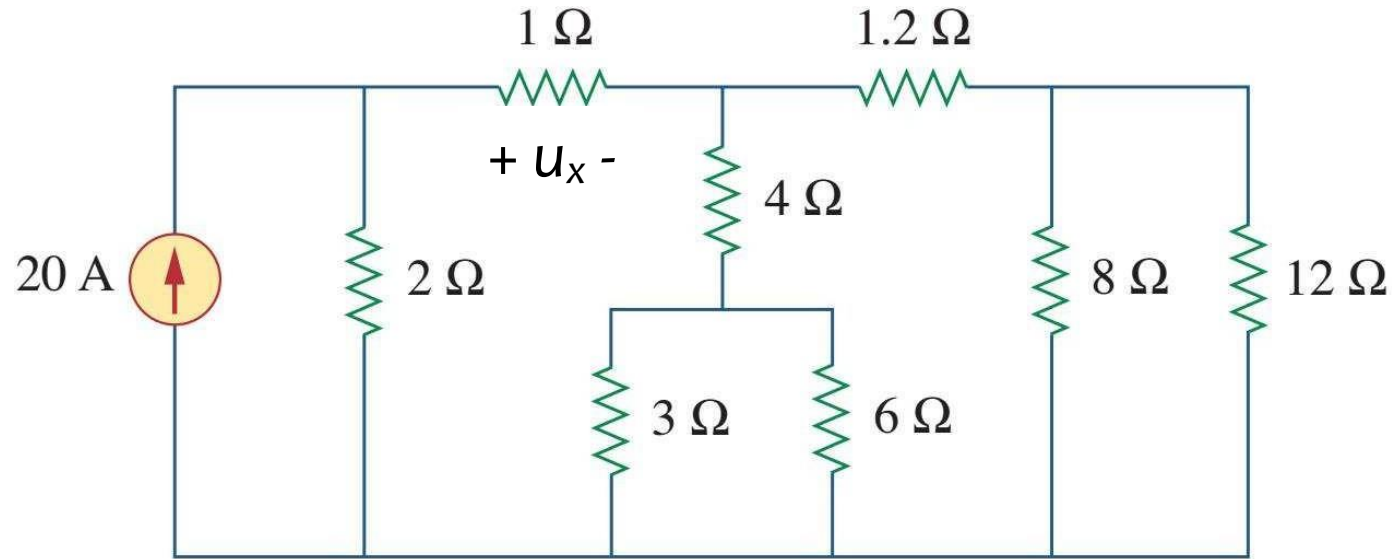


Fig 1.5.6: Circuit for Example 1.5.2

by: Dr. Prosper NDIZIHIWE, INES Ruhengeri